



①

A	B	C	D	Display?
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	A
1	0	1	1	B
1	1	0	0	C
1	1	0	1	D
1	1	1	0	E
1	1	1	1	F

②

Display	A	B	C	D	E	F	G
0	1	1	1	1	1	1	0
1	0	1	1	0	0	0	0
2	1	1	0	1	1	0	1
3	1	1	1	1	0	0	1
4	0	1	1	0	0	1	1
5	1	0	1	0	1	1	1
6	1	0	1	1	1	1	1
7	1	1	1	0	0	0	0
8	1	1	1	1	1	1	1
9	1	1	1	0	0	1	1

③

J	K	Display
0	0	H
0	1	I
1	0	G
1	1	H

④

Display	A	B	C	D	E	F	G
A	1	1	1	0	1	1	1
B	0	0	0	1	1	0	1
C	1	0	0	1	1	1	1
D	0	0	1	1	1	0	0
E	0	1	1	1	1	1	0
F	0	0	1	1	1	0	1
G	0	0	1	0	1	1	1
H	0	1	1	0	1	1	1
I	0	0	0	0	1	1	0
J	1	0	0	1	1	1	1

DESIGNED BY:

DATE

WITNESSED BY:

DATE



**PROPRIETARY  
INFORMATION**

 All information is the property of,  
and solely owned by the Designer.





- ④ a. Segment A is on b. it shows nothing *p-10*  
⑤ a. Segment A is off b. it shows nothing *1010<sub>2</sub> - 1111<sub>2</sub> invalid*  
⑥ a. it is glitching b. yes *K-20*  
*CK - LS48 high output, seg on*  
*CA - LS47 Low output, seg on*  
C. putting NOR gates on the outputs of OA, ~~OB~~ OB, etc. to show decimal numbers

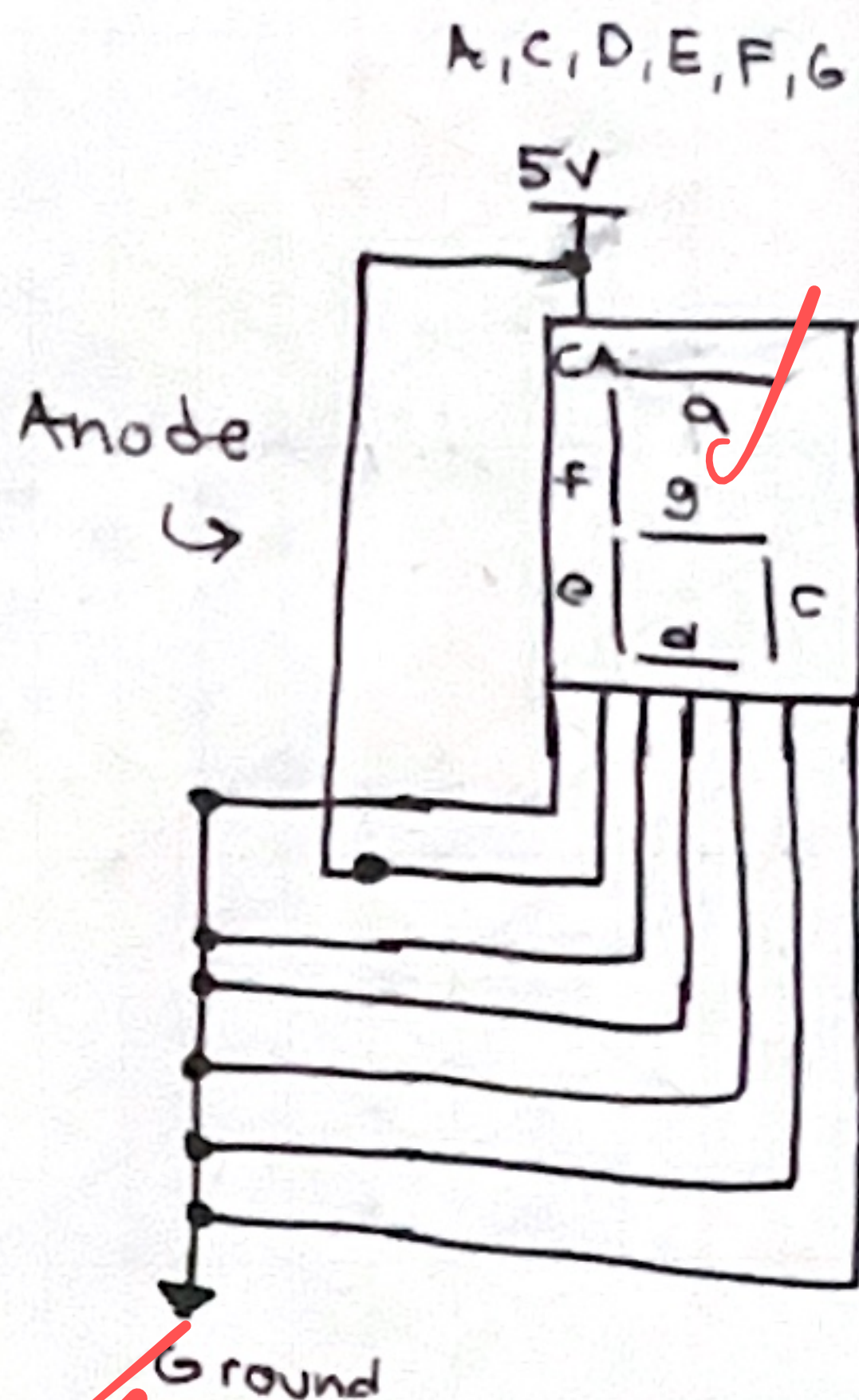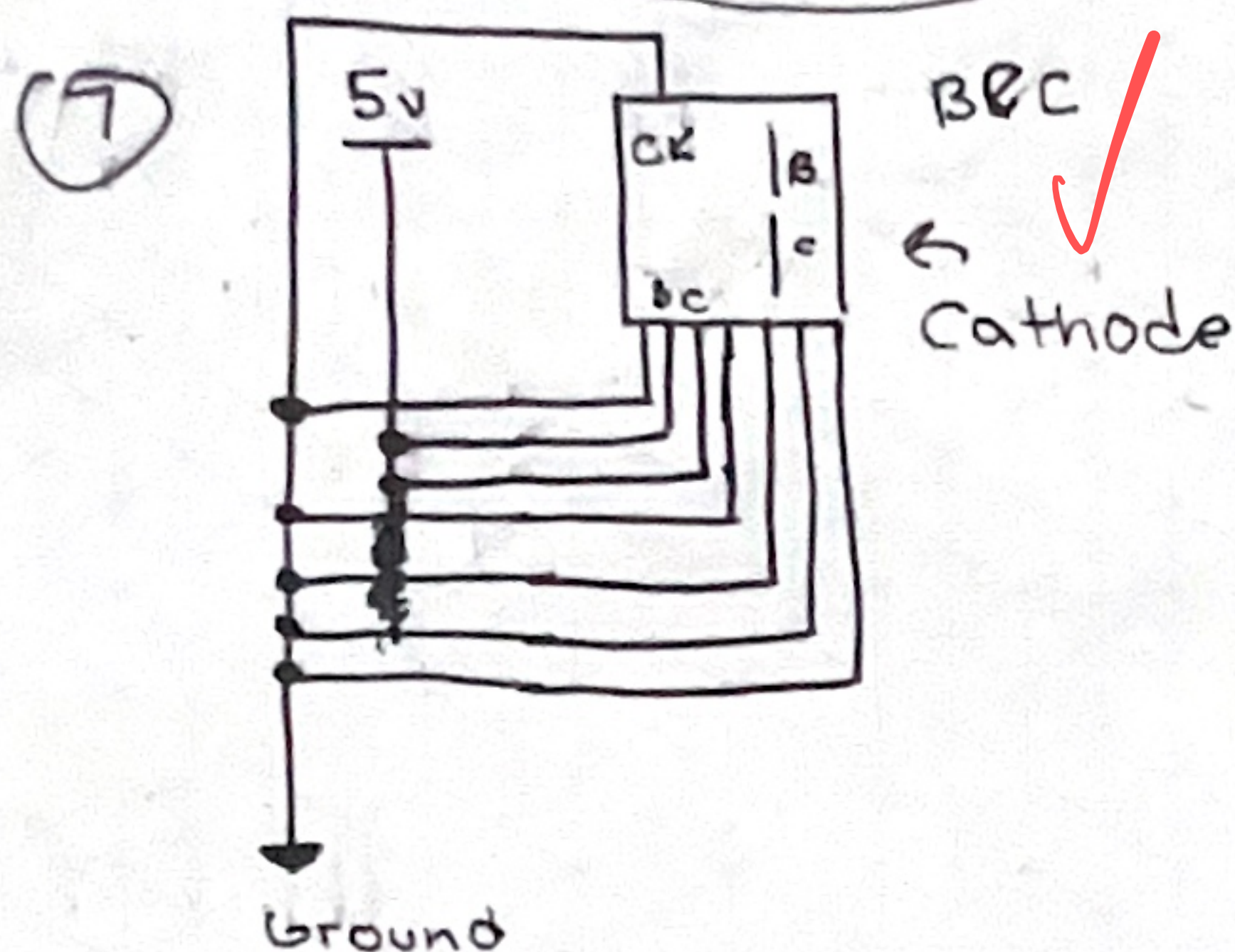Conclusion questions

- ⑧ COOL, BIG, EGG, BEE, See  
⑨ Check for correct polarity, proper wiring, current limiting resistors, power supply issues, and visibility

*could be inverted*

*30*

DESIGNED BY:

DATE

WITNESSED BY:

DATE

**PROPRIETARY  
INFORMATION**All information is the property of,  
and solely owned by the Designer.